

Clock Skew and Short Paths Timing

Clock Skew

Differences in clock signal arrival times across the chip are called clock skew. It is a fundamental design principle that timing must satisfy register setup and hold time requirements. Both data propagation delay and clock skew are parts of these calculations. Clocking sequentially-adjacent registers on the same edge of a high-skew clock can potentially cause timing violations or even functional failures. Figure 1 shows an example of sequentially-adjacent registers, where a local routing resource has been used to route the clock signal. In this situation, a noticeable clock skew is likely.

In Figure 1, all registers are clocked at the same edge, but the arrival time of the edge is different at each register. Figure 2 indicates an example of the clock skew for the circuit shown in Figure 1.

 


Figure 1 • Sequentially Adjacent Registers with Clock Skew

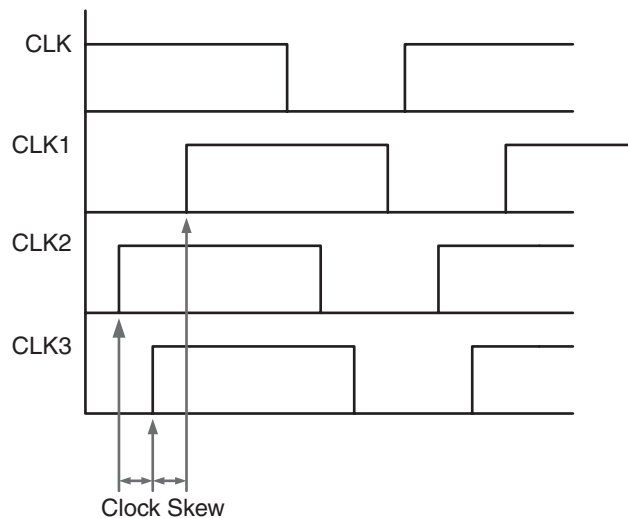


Figure 2 • Clock Arrival Time Fluctuations in the Circuit of Figure 1

Clock Skew and the Short Path Problem

The problem of short data paths in the presence of clock skew is very similar to hold-time violations in flip-flops. The problem arises when the data propagation delay between two adjacent flip-flops is less than the clock skew. [Figure 3](#) shows an example of a simple circuit with waveforms to illustrate a short-path problem.

In [Figure 3](#), since the same clock edge arrives at the second flip-flop later than the new data, the second flip-flop output switches at the same edge as the first flip-flop and with the same data as the first flip-flop. This will cause U2 to shift the same data on the same edge as U1, resulting in a functional error.

The next sections discuss how to analyze clock skew and short paths and identify potential problems.

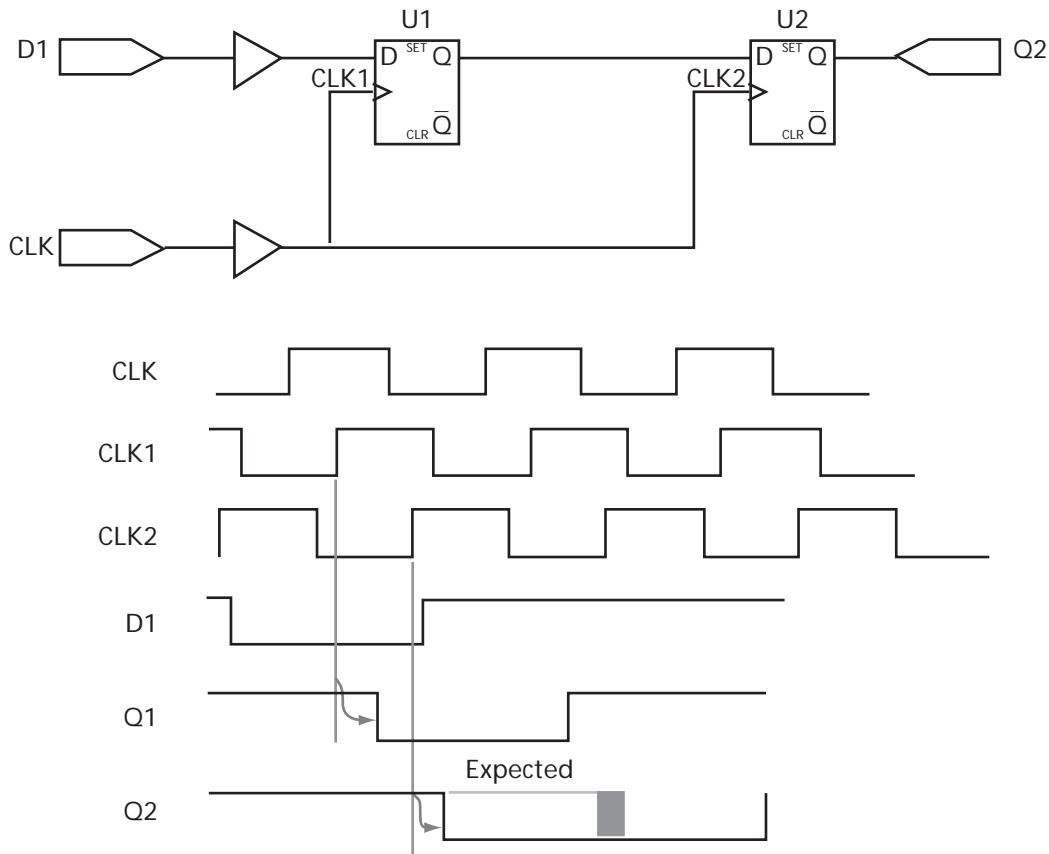


Figure 3 • A Simple Circuit with Clock Skew and Sample Waveforms

How to Measure Clock Skew

The first step in coping with clock skew problems is to measure the clock skew. Users should perform a static timing analysis of the design after place-and-route to determine the amount of clock skew.

For SX-A, RTSX-S, eX, Accelerator, RTAX-S, ProASIC and ProASIC^{PLUS} (and any other new Actel devices) Timer can generate a setup and hold time violation report for register-to-register paths in the same clock domain. Users can generate the report by opening Timer from Actel Designer software and going to File -> Tool -> Report Violation.

The timing violation report is only valid if the user has specified one or more clock constraints. If the design clocks are not constrained, the report will be empty. The timing violation report has four sections as follows:

- Header: This section contains software version, design name, operating condition, device type, speed grade and Timer preferences.
- Clock Constraint Violation: This section reports the critical paths limiting any clock frequency constraint set in the General tab window.
- Max Delay Constraint Violation: This section reports the critical paths that are limiting any Max Delay constraint set in the Timer Path tab window.
- Min Delay Constraint Violation: In this section, short data paths that are susceptible to hold-time violations are listed.

In the timing violation report, the skew of the clock network is taken into account in calculating the slack. The report is sorted by slack for each section; a negative slack indicates a violation.

The timing violation report is created based on the operating conditions set in the timer preferences. Therefore, to examine the long data paths versus any clock or Max Delay Constraint, the user should export the report while the timer preferences are set to worst case/long paths. On the other hand, to identify all the possible hold-time violations, the report should be created while the timer preferences are set to best case/short paths. Users should note that after each change in the operating conditions in the Timer window, the "calculate delays" option should be selected before exporting the timing violation report.

Timer, the static timing analysis tool in Actel's Designer software, can add specific path sets, which include the paths from the clock source (external or internal) to the CLK input of the registers. Note that the maximum difference of the path delays reflects the worst-case skew of the clock network. However, this is not necessarily the worst-case clock-skew/short-path relationship since all the registers on the clock network may not be sequentially adjacent.

In Designer versions beginning with R1-2003 SP1, the Timer tool will calculate and report the clock skew of each register-to-register path (the skew between the source and sink registers). This is done in the expanded path window for each path. In previous Designer software releases, one basic set of paths needed to be added to the Timer path sets to extract the clock skew. The set should include all the paths starting (source) from the clock signal driver and ending (sink) in all the registers driven by that clock. The path can be defined through the GUI using filter keywords or through the Timer keywords using the "Advanced" tab of the "Add Path Set" GUI. For more information on the Timer Keywords and GUI, please refer to the *Timer user's guide* and online help. As an example, consider an external clock, named "CLK_IN," driving a set of registers in a design. The following keywords will define the source and sink points of the desired paths to identify the clock skew:

- From: \$inputs(CLK_IN) To: \$clocks(CLK_IN)[*CLK]

The above keywords will set up a path set from the CLK_IN input to the CLK ports of all the relevant flip-flops.

Since this document discusses the short-path problems, the user MUST set the Timer preferences (File -> Preferences) to Best Case in order to view the shortest paths ([Figure 4 on page 4](#)).

Clock Skew and Short Path Analysis

As mentioned earlier, clock skew and short-path problems emerge when the data propagation path delay between two sequentially adjacent flip-flops is less than the clock skew between the two. Figure 5 is a general diagram of the delay blocks in a sample circuit.

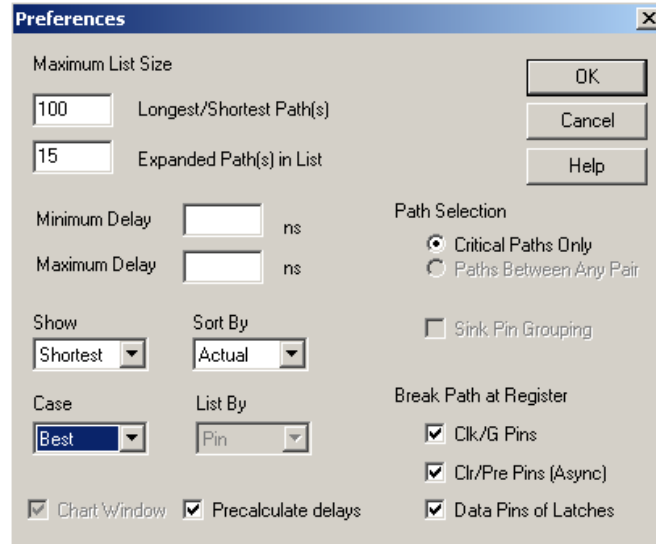


Figure 4 • Setting Shortest Paths and Best Case in Timer

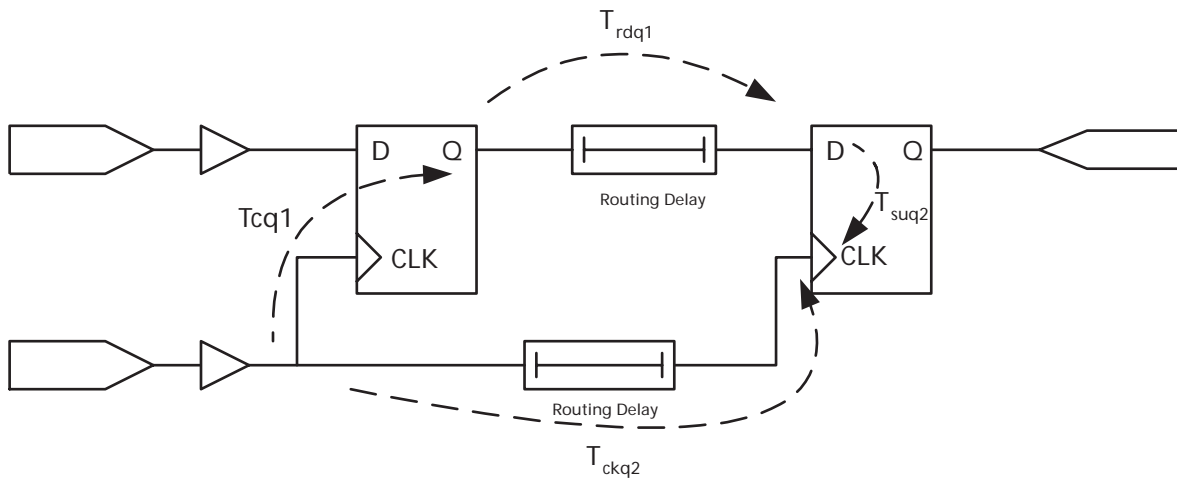


Figure 5 • General Delay Blocks in a Simple Circuit

The delays in Figure 5 on page 4 are as follows:

- t_{CQ1} : The clock to out delay of the first flip-flop
- t_{RDQ1} : The propagation delay from the output of the first flip-flop to the input of the second one
- t_{CK2} : The clock arrival time at the second flip-flop minus the clock arrival time at the first flip-flop

The short-path problem will definitely emerge in this circuit if

EQ 1

$$t_{CK2} > t_{CQ1} + t_{RDQ1} - t_{HOLD2}$$

Where t_{HOLD2} is the hold-time requirement of the sink flip-flop. The regions are illustrated in Figure 6.

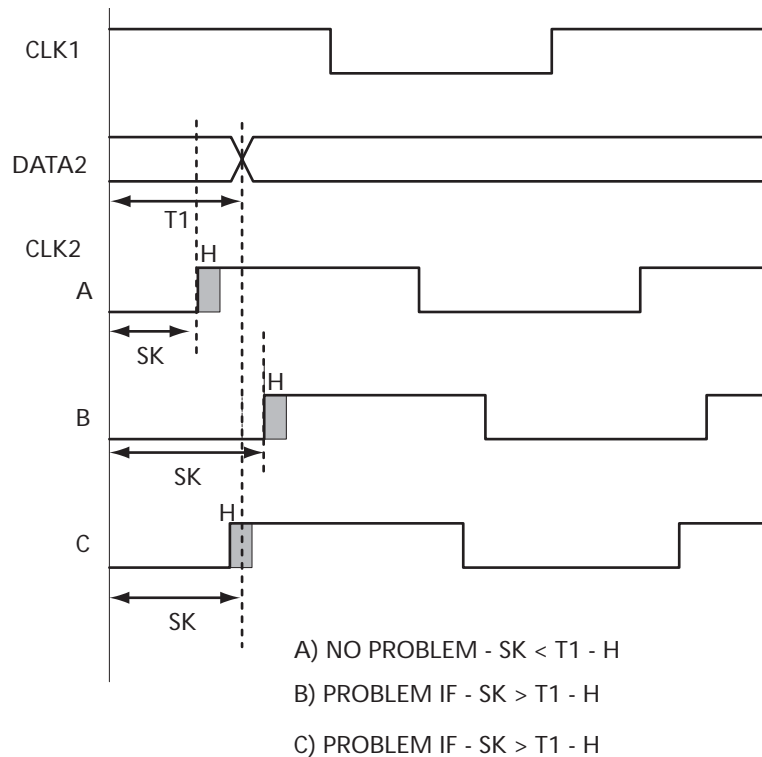


Figure 6 • Illustration of the Short-Path Problem

In practice, it is best to use EQ1 to identify potential problems and violations.

Therefore, in order to identify the paths with the problem, the user needs to extract the clock skew (e.g. t_{CK2}) and the short-path delays (e.g. $t_{CQ1} + t_{RDQ1} - t_{HOLD2}$).

In the "How to Measure Clock Skew" section on page 3 the clock skew extraction method was discussed.

Minimizing the Clock Skew

The short-path problem is created by the existence of unacceptably large clock skew. Therefore, minimizing (i.e., nearly removing) the clock skew is the best approach to reduce the risk of short-path problems. Actel devices offer global routing resources, which reduce skew.

If there are any free global resources available on the device, users should assign their clock signals to these resources. Maintaining the clock skew at a value less than the smallest register-to-register delay in the design by using low-skew global resources will improve the robustness of the design against any short-path problems. The hardwired and quadrant clock resources (HCLK, QCLKA, QCLKB, QCLKC and QCLKD) in A54SX-A, RT54SX-S as well as global resources (GL) in Actel's Flash FPGAs are designed to prevent design errors due to clock skew. The skew will always be less than the shortest possible data path. Routed global networks, such as CLKA and CLKB, offer reduced clock skew. However, Actel recommends adding design margin since all possible configurations of routing and clock loading cannot be accurately characterized. For more information on the available global resources on each device family, please refer to the following documents provided on the Actel website:

- [Global Clock Networks in Actel Antifuse Devices](#)
- [Using Global Resources in Axcelerator Family](#)
- [Efficient Use of ProASIC Clock Trees](#)

Actel's Designer software version R1-2003 with Service Pack 1 and later releases support clock skew analysis for RTSX-S, eX, ProASIC, ProASIC^{PLUS}, and Axcelerator. For future software updates, please refer to the software or service pack release notes.

Design Techniques for Limited Global Resources

In cases where designs include multiple clock domains, there may not be enough low-skew global resources in the targeted FPGA for all the external/internal clock signals. Therefore, regular routing resources and buffers are used to build clock trees for the clock network. Since using the regular nets for clock signals may cause noticeable clock skew, the user should employ specific design techniques to reduce or eliminate the risk of a short data path problem. The following sections are a few well-known design techniques to make designs more robust against clock skew.

Add Delay in Data Path

Figure 5 on page 4 suggests that increasing the t_{RDQ1} (routing delay in the data path), and consequently, increasing the total delay of the data path to a value greater than the clock skew, will eliminate the short path problem.

To insert delay in the data path, the user can employ BUFD or INVD macros from Actel's library as delay elements. For more information on usage of these macros please refer to the [Using BUFD and INVD Delay Macros](#) application note.

Figure 7 on page 7 shows a simple example of BUFD insertion in the data path.

The amount of the inserted delay (number of BUFD or INVD macros) in the data path should be large enough so that the data path delay becomes sufficiently greater than the clock skew. Manual placement of the buffer can significantly improve the added delay. Actel recommends positioning the buffer so that it is not adjacent to either the source or receiving register. This prevents using fast routing tracks.

Clock Reversing

Clock reversing is another approach to get around the problem of short data paths and clock skew. In this method, the clock signal arrives at the clock port of the sink (receiving) register sooner than the source (transmitting) register. Therefore, the receiving (sink) register will clock in the transmitting (source) value before the transmitting register receives its clock edge. Figure 8 on page 7 shows a simple example of implementing the clock reversing approach.

The BUFD macro, shown in Figure 8, adds delay to the clock driving the source register. When sufficient delay is inserted, the receiving register will receive the active-clock edge before the source register.

The clock reversing method will not be effective in circular structures such as Johnson counters and Linear Feedback Shift Registers (LFSRs), because it is not possible to define the sink register explicitly. Figure 9 on page 8 shows an example of a circular structure with clock reversing interconnection.

Figure 9 on page 8 shows that the short-path problem exists between flip-flops U1 and U3.

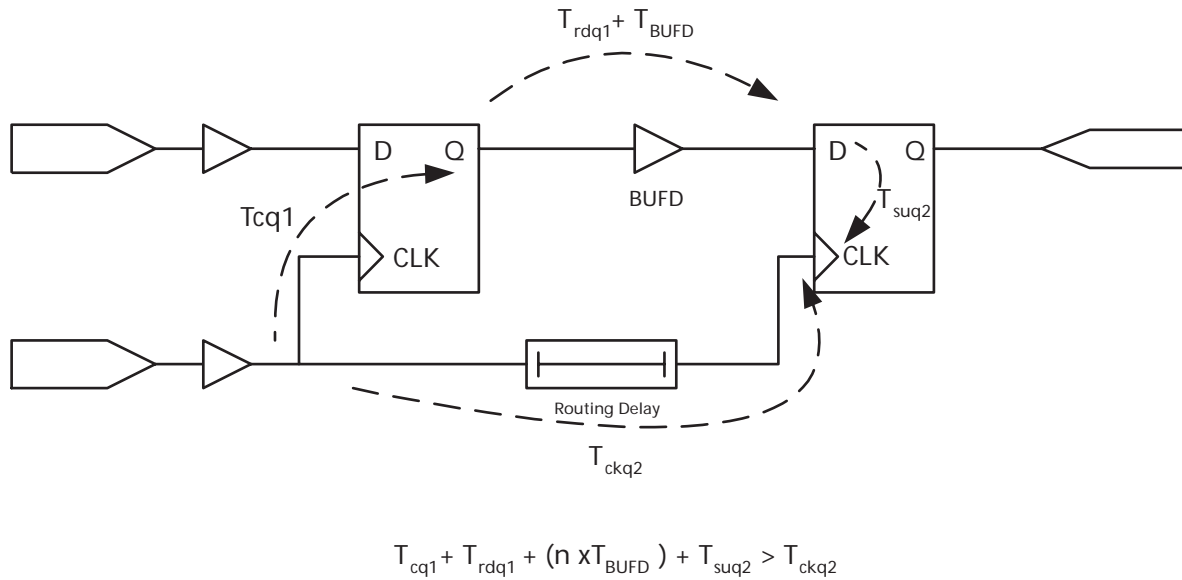


Figure 7 • BUFD Delay Insertion in the Data Path

 


Figure 8 • Clock Reversing Methodology

Alternate Phase Clocking

One of the known methodologies to avoid clock skew issues is alternate-phase clocking. The following are the most common methods of alternate phase clocking:

- Clocking on alternate edges
- Clocking with two phases

In the first method, sequentially adjacent registers are clocked on the opposite edges of the clock. Part A of Figure 10 shows an example of alternate sequentially adjacent registers being clocked on opposite edges. As can be seen in part A of Figure 10, this method provides a short path-clock skew margin of about one-half clock cycle for clock skew.

 


Figure 9 • Clock Reversing in a Circular Structure

 


Figure 10 • Alternative Edge/Phase Clocking

Part B of [Figure 10 on page 8](#) shows a set of adjacent registers, which are alternately clocked on two different phases of the same clock. In this case, between each two adjacent registers, there is a safety margin approximately equal to the phase difference of the two phases.

The risk of the short-path problem is extremely low in these cases since in each data path there is at least one register (clocking on the alternate edge/phase) in the data path delay. [Figure 11](#) shows an example of the signal waveforms in part A of the [Figure 10 on page 8](#) circuit.

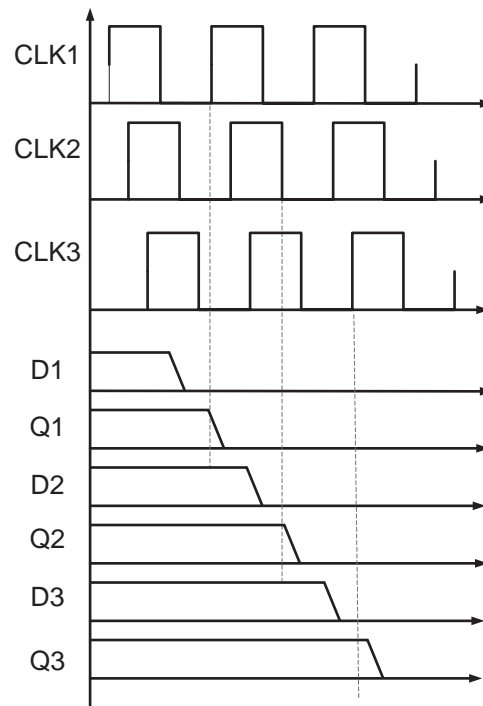


Figure 11 • Signal Propagation for the Circuit in [Figure 10 on page 8](#)

The user should note that the usage of alternate-phase clocking may require completely different clock constraints on the original clock signal. For example, in the case of clocking on alternate edges, the new constraint on the clock frequency will be half the original frequency since the adjacent registers are clocked on opposite edges of the same clock cycle. [Figure 12 on page 10](#) shows another example of opposite-edge clocking. In this example, the up-counter increments its output at the falling edge of the clock while the updated value is registered to the next level of logic on the rising edge of the clock.

Ripple Structures

In a ripple structure, each register output drives the next register clock port. Therefore, the sink register will not clock unless the source (driver) register is toggled. [Figure 13 on page 10](#) shows an example of a three-bit ripple-down and ripple-up counter.

The output of each counter register drives the clock port of the next register instead of its data input port. This will eliminate the clock skew since the registers do not toggle on the same clock. The first register is clocked on the positive edge of the CLK signal and the second- and third-stage registers are clocked on the positive edge of the output of the previous register. [Figure 14 on page 10](#) shows sample waveforms of the three-bit ripple counter outputs.

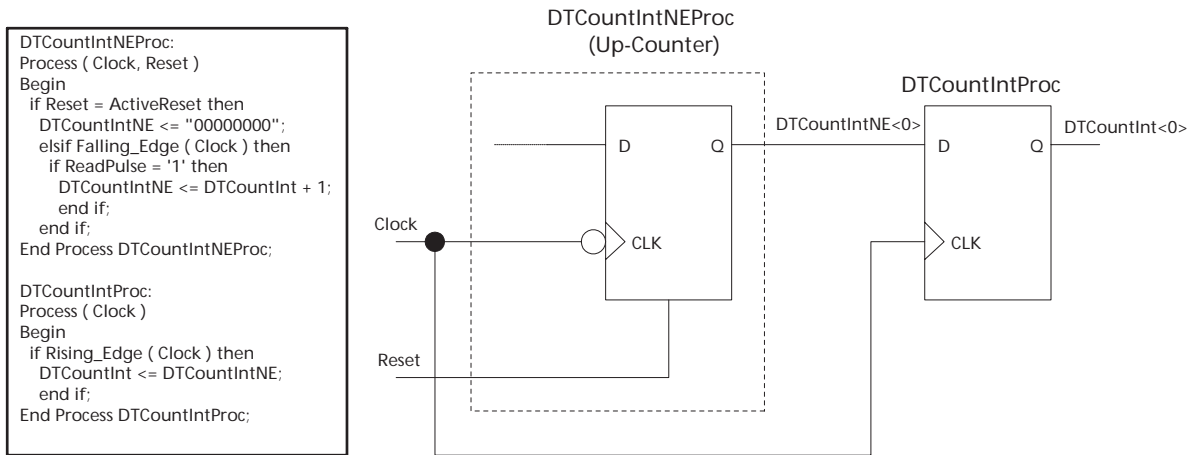


Figure 12 • Counter Design With Opposite-Edge Clocking

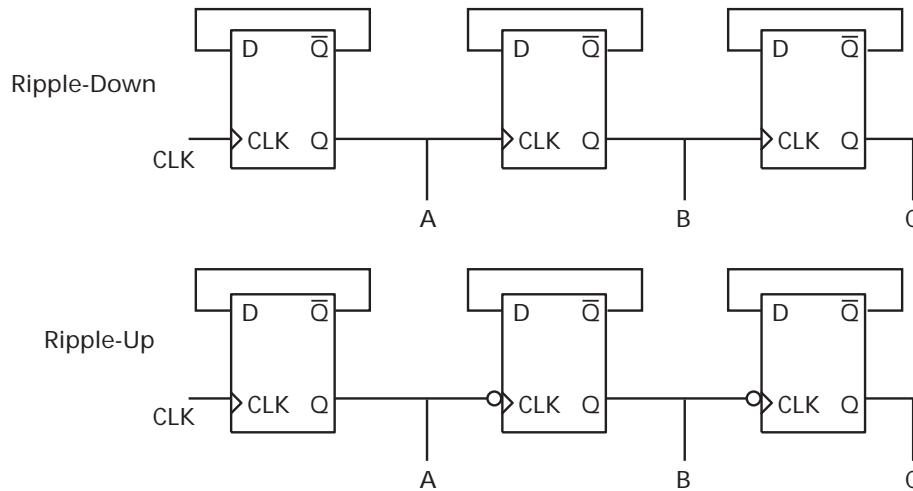


Figure 13 • Three-Bit Ripple Counter

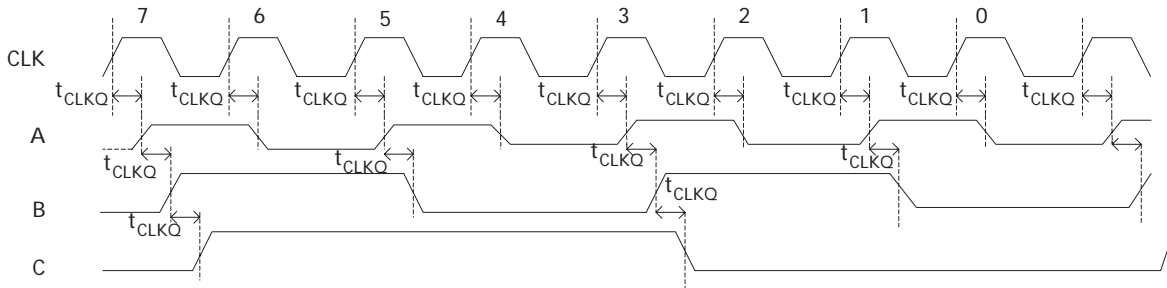


Figure 14 • Three-Bit Ripple Counter Input and Outputs

Insight Into Minimum Delays

Design engineers tend to push the speed of the devices IC manufacturers provide, and emphasis is placed on improving the performance of devices through innovative design techniques and careful timing analysis. Maximum delays in the worst-case operating conditions are used to calculate the fastest speed at which a device can operate. Therefore, all device manufacturers screen devices to ensure the maximum delays are equal to or better than the posted performance. Manufacturers also tend to provide devices that are guaranteed to exceed the standard timing. Actel gives devices a speed grade rating such as -1, -2, or in some cases -3 for the fastest possible device. Since great emphasis is placed on satisfying the maximum delay values, manufacturers do not typically specify the minimum delay values. In other words, manufacturers will guarantee devices to be faster than X, but do not guarantee that devices will be slower than Y.

This poses an interesting problem for designers who must satisfy timing parameters for both maximum and minimum delays. Since maximum delays are guaranteed, normal delay extraction and timing analysis will highlight any potential timing issues for maximum delays. Some designers address the minimum delay issue by using the minimum delays from the fastest possible speed grade. Some multiply a derating factor to the extracted data to ensure added margin. While both of the above techniques improve the reliability of the design, the best ways to avoid functional errors are to use design techniques that do not depend on the minimum delay values for proper functionality OR use dedicated hardwired resources such as the HCLK network in SX-A and RTSX-S devices. Several of the design techniques were outlined in the previous section, while the HCLK, QCLK and GL networks are designed to be free of errors due to clock skew.

Conclusion

The difference in the arrival times of the clock signals between two sequentially-adjacent registers (clock skew) may cause the design to malfunction when the data paths are short. The simplest method to help prevent the short data path problem is to minimize the clock skew by using the low-skew global routing resources for clock signals. Actel devices provide various types of global routing resources which significantly reduce skew.

For designs in which there are a large number of clock domains, the user may run out of global routing resources and be forced to build a clock tree using regular nets to distribute a clock signal. This will introduce clock skew and possibly short data path problems. Various design techniques, such as inserting data path delays or clock reversing, can be used to reduce the risk of the design malfunction caused by clock skew. However, due to the limitations and shortcomings of each design technique, Actel recommends that users fully exploit the available global routing resources of the selected device.

Actel's Designer software version R1-2003 with service pack 1 (and later releases) support clock skew analysis for supported FPGA families. For future software updates, please refer to the Designer software or service pack release notes.

Related Documents

Application Notes

Global Clock Networks in Actel Antifuse Devices

<http://www.actel.com/appnotes/GlobalClk.pdf>

Using Global Resources in Axcelerator Family

http://www.actel.com/appnotes/AX_Global_Resources.pdf

Efficient Use of ProASIC Clock Trees

<http://www.actel.com/appnotes/clocktree.pdf>

User's Guide

Timer user's guide

<http://www.actel.com/docs/R1-2002/timer.pdf>

List of Changes

Previous Version	Changes in Current Version 51900001-1/3.04*	Page
51900001-0/1.03	The "Clock Skew" section on page 1 was updated.	page 1
	The "Clock Skew and the Short Path Problem" section on page 2 was updated.	page 2
	The "How to Measure Clock Skew" section on page 3 was updated.	page 3
	Figure 6 on page 5 was updated.	page 5
	The "Insight Into Minimum Delays" section on page 11 is new.	page 11

Note: * The part number is located on the last page of the document.

Actel and the Actel logo are registered trademarks of Actel Corporation.
All other trademarks are the property of their owners.



<http://www.actel.com>

Actel Corporation

2061 Stierlin Court
Mountain View, CA
94043-4655 USA

Phone 650.318.4200
Fax 650.318.4600

Actel Europe Ltd.

Dunlop House, Riverside Way
Camberley, Surrey GU15 3YL
United Kingdom

Phone +44 (0) 1276 401 450
Fax +44 (0) 1276 401 490

Actel Japan

EXOS Ebisu Bldg. 4F
1-24-14 Ebisu Shibuya-ku
Tokyo 150 Japan

Phone +81.03.3445.7671
Fax +81.03.3445.7668

Actel Hong Kong

39th Floor, One Pacific Place
88 Queensway, Admiralty
Hong Kong

Phone 852.227.35712
Fax 852.227.35999